

Tutorial - 3

1)

(i) For SR latch

$$Q(n+1) = S + R' Q(n)$$

Here

$$S = A \oplus B = AB' + A'B$$

$$R = B$$

So,

$$Q(n+1) = AB' + A'B + B'Q(n)$$


(ii) Char Table

| A | B | $Q(n)$ | $Q(n+1)$ |
|---|---|--------|----------|
| 0 | 0 | 0      | 0        |
| 0 | 0 | 1      | 1        |
| 0 | 1 | 0      | 1        |
| 0 | 1 | 1      | 1        |
| 1 | 0 | 0      | 1        |
| 1 | 0 | 1      | 1        |
| 1 | 1 | 0      | 0        |
| 1 | 1 | 1      | 0        |

## Excitation Table

| $Q(n)$ | $Q(n+1)$ | A | B |
|--------|----------|---|---|
| 0      | 0        | 0 | 0 |
| 0      | 1        | 0 | 1 |
| 1      | 0        | 1 | 1 |
| 1      | 1        | 0 | 0 |
|        |          | 1 | 0 |
|        |          | 0 | 1 |

2)

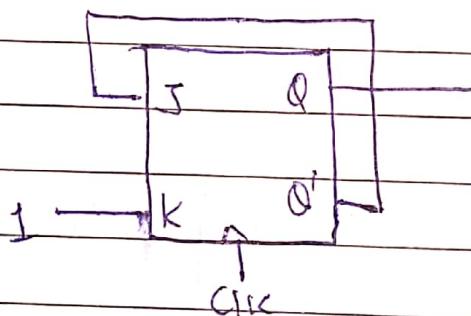

$$J = Q', \quad K = 1$$

Flip flop is initially closed  $\Rightarrow Q = 0$

1<sup>st</sup> Clock pulse  $\Rightarrow J=1, K=1, Q(n)=0 \Rightarrow Q(n+1)=1$   
(CP)

2<sup>nd</sup> CP  $\Rightarrow J=0, K=1, Q(n)=1 \Rightarrow Q(n+1)=0$

3<sup>rd</sup> CP  $\Rightarrow J=1, K=1, Q(n)=0 \Rightarrow Q(n+1)=1$

4<sup>th</sup> CP  $\Rightarrow J=0, K=1, Q(n)=1 \Rightarrow Q(n+1)=0$

5<sup>th</sup> CP  $\Rightarrow J=1, K=1, Q(n)=0 \Rightarrow Q(n+1)=1$

6<sup>th</sup> CP  $\Rightarrow J=0, K=1, Q(n)=1 \Rightarrow Q(n+1)=0$

3) Initially

Assume: Clear state

$$Q=0$$

$$\bar{Q}=1$$

For D flip flop  $\Rightarrow Q(n+1)=D$

$\begin{cases} Q(n)=0 \end{cases} \Rightarrow \begin{cases} T=0, \text{ So, } D=0 \Rightarrow Q(n+1)=0 \end{cases}$

$\begin{cases} Q(n)=1 \end{cases} \Rightarrow \begin{cases} T=1 \Rightarrow D=1 \Rightarrow Q(n+1)=1 \end{cases}$

$\begin{cases} Q(n)=1 \end{cases}$


$\begin{cases} T=0, D=1 \end{cases} \Rightarrow Q(n+1)=1$

$\begin{cases} T=1 \end{cases} \Rightarrow D=0 \Rightarrow Q(n+1)=0$

| T | Q(n) | Q(n+1) |
|---|------|--------|
| 0 | 0    | 0      |
| 0 | 1    | 1      |
| 1 | 0    | 1      |
| 1 | 1    | 0      |

Same as  
T flip flop  
Truth Table

4)

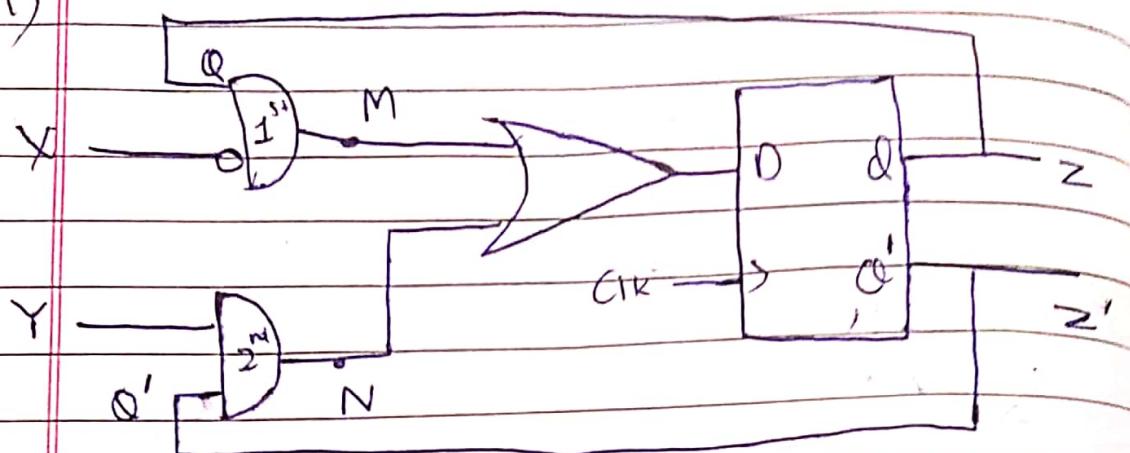

~~Put  $X = K$  &  $Y = J$~~

Using 1<sup>st</sup> And gate we get  $M = K'Q(n)$

& 2<sup>nd</sup> And gate we get  $N = JQ'(n)$

So,

$$D = JQ'(n) \rightarrow K'Q(n) \quad \text{---(1)}$$

Now,

As we know is D flip-flop

$$D = Q(n+1) \quad \text{---(2)}$$

using (1) & (2)

$$Q(n+1) = JQ'(n) + K'Q(n)$$

which is characteristic equation of

JK flip flop

Hence Proved

- 5)  $XY = 00 \Rightarrow$  Change state with CP.  
 $XY = 01 \Rightarrow Q = 1$  with CP  
 $XY = 10 \Rightarrow Q = 0$  with CP  
 $XY = 11 \Rightarrow$  Change state with CP

a) So, According to This

| X | Y | $Q(n+1)$                           |
|---|---|------------------------------------|
| 0 | 0 | <del><math>Q'</math></del> $Q'(n)$ |
| 0 | 1 | 1                                  |
| 1 | 0 | 0                                  |
| 1 | 1 | $Q'(n)$                            |

| $Q(n)$ | X | Y | $Q(n+1)$ |
|--------|---|---|----------|
| 0      | 0 | 0 | 1        |
| 0      | 0 | 1 | 1        |
| 0      | 1 | 0 | 0        |
| 0      | 1 | 1 | 1        |
| 1      | 0 | 0 | 0        |
| 1      | 0 | 1 | 1        |
| 1      | 1 | 0 | 0        |
| 1      | 1 | 1 | 0        |

Excitation Table

| $Q(n)$ | $Q(n+1)$ | X | Y |
|--------|----------|---|---|
| 0      | 0        | 1 | 0 |
| 0      | 1        | 0 | 0 |
|        |          | 0 | 1 |
|        |          | 1 | 1 |
| 1      | 0        | 0 | 0 |
|        |          | 1 | 0 |
|        |          | 1 | 1 |
| 1      | 1        | 0 | 1 |

(ii)  $\begin{array}{c} XY \\ \hline Q(n) \end{array}$

|   | 00 | 01 | 11 | 10 |
|---|----|----|----|----|
| 0 | 1  | 1  | 1  | 0  |
| 1 | 0  | 1  | 0  | 0  |

$$Q(n+1) = Q'(n) X' + Q'(n) Y + X' Y$$

$$Q(n+1) = (X' + Y) Q'(n) + X' Y$$

By characteristic equation of JK flip flop

$$Q(n+1) = J Q'(n) + K' Q(n) \quad -(1)$$



$$Q(n+1) = (X' + Y) Q(n) + X'Y(Q(n) + Q'(n))$$


$$Q(n+1) = (X' + Y + X'Y)^{Q(n)} + X'Y Q'(n)$$

(2)

Comparing (1) & (2)

$$J = (X' + Y + X'Y) \cancel{Q(n)}$$

$$K = X'Y$$

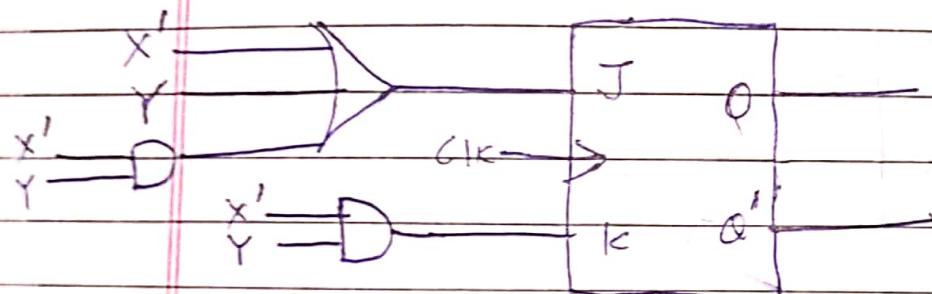


### 6) a) Excitation Table

| $Q(n)$ | $Q(n+1)$ | A | B |
|--------|----------|---|---|
| 0      | 0        | 1 | 0 |
| 0      | 1        | 1 | 1 |
| 1      | 0        | 0 | 0 |
| 1      | 1        | 0 | 1 |

| $Q(n)$ | A | B | $Q(n+1)$ | T |
|--------|---|---|----------|---|
| 0      | 0 | 0 | 1        | 1 |
| 0      | 0 | 1 | 1        | 1 |
| 0      | 1 | 0 | 0        | 0 |
| 0      | 1 | 1 | 0        | 0 |
| 1      | 0 | 0 | 0        | 1 |
| 1      | 0 | 1 | 1        | 1 |
| 1      | 1 | 0 | 0        | 0 |
| 1      | 1 | 1 | 1        | 0 |


| $Q(n)$ | AB | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|----|
| 0      | 1  | 1  | 0  | 0  |    |
| 1      | 1  | 1  | 0  | 0  |    |

$$T = A'$$

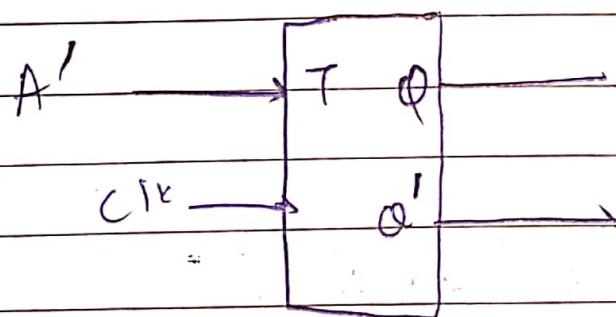

7)

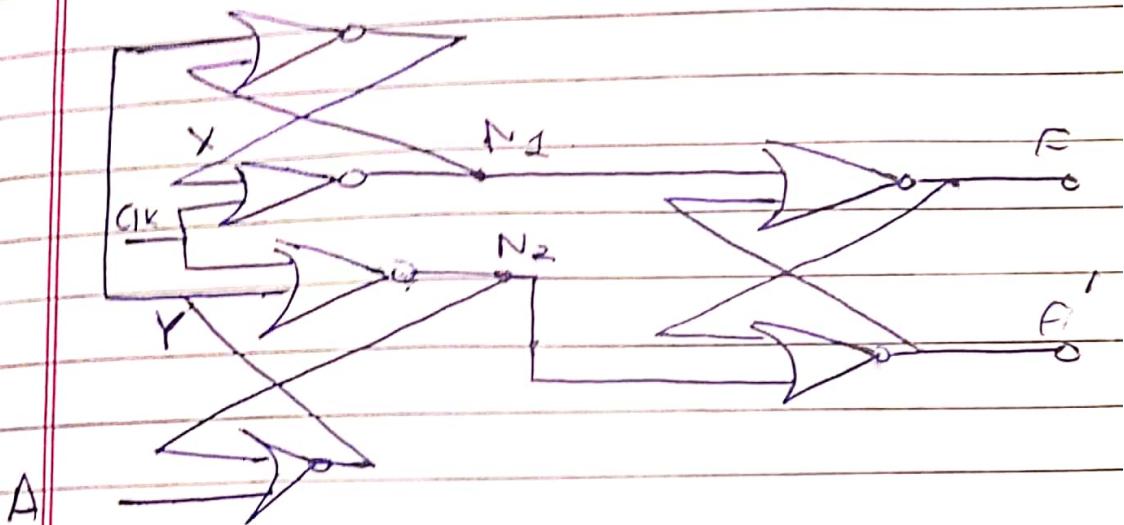a)  $C_{IK} = 1 \quad A \Rightarrow 0 \text{ to } 1$



XOR Truth table

| X | Y | Z |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

If any input is '1'  
 $Z = 0$

So, using above concept

Before 'A' was charge

if  $C_{IK} = 1 \quad \& \quad A = 0$

$$C_{IK} = 1 \Rightarrow N_1 = 0, N_2 = 0$$

$$\text{Now, } N_1 = 0 \Rightarrow X = 0 \quad \& \quad F_{(n)} = 0$$

Now,

$$F_{(n)} = 0 \quad \& \quad N_2 = 0 \Rightarrow F'_{(n)} = 1$$

Now change A from 0 to 1

~~A~~ If  $C_{IK} = 1$  &  $A = 1$  [A charged from 0 to 1]

$C_{IK} = 1 \Rightarrow N_1 = 0, N_2 = 0$

Now,

$N_1 = 0 \Rightarrow X = 0$  & ~~F~~  $F(n+1) = 0$

Now,

$F(n+1) = 0$  &  $N_2 = 0 \Rightarrow F'(n+1) = 1$

So, By comparing before A was charged & after it  
we get

$$F(n) = f(n+1)$$

b) Before  $C_{IK}$  was charged

$A = 1$  &  $C_{IK} = 1$

$C_{IK} = 1 \Rightarrow N_1 = 0, N_2 = 0$

Now,

$N_1 = 0 \Rightarrow X = 0$  &  $F(n) = 0$

Now,

$F(n) = 0$  &  $N_2 = 0 \Rightarrow F'(n) = 1$

After  $C_{IK}$  charged from '1' to '0'

$C_{IK} = 0$  &  $A = 1$

$$\text{if } A = 1 \Rightarrow Y = 0$$

Now,

$$Y = 0 \quad \cancel{\text{& } \text{clk} = 0} \quad \& \text{ clk} = 0 \Rightarrow N_2 = 1$$

Now,

$$N_2 = 1 \Rightarrow F'(n+1) = 0$$

Now

$$Y = 0 \rightarrow \& (N_1 \text{ initial value before } = 0)$$

So,  $\text{clk changed}$

$$X = 1$$

& Now

$$X = 1 \Rightarrow N_1 = 0$$

$$N_1 = 0 \& F'(n+1) = 0 \Rightarrow F(n+1) = 1$$

So,

Comparing after & before CLK changes  
Value we get

$$F(n) = F'(n+1)$$

(c) Before A was charged :

$$\text{Clk} = 0 \quad \& \quad A = 1$$

Now  $A = 1 \Rightarrow Y = 0$

$$Y = 0 \quad \& \quad \text{Clk} = 0 \Rightarrow N_2 = 1$$

Now

$$N_2 = 1 \Rightarrow f'(n) = 0$$

Now

$$Y = 0 \quad \& \quad \left( \begin{array}{l} N_2 \text{ value} = 0 \\ \text{initially} \end{array} \right) \Rightarrow X = 1$$

Now

$$X = 1 \Rightarrow N_1 = 0$$

$$N_1 = 0 \quad \& \quad f'(n) = 0 \Rightarrow f(n) = 1$$

Now A is charged

$$\text{Clk} = 0 \quad \& \quad A = 0$$

$$(\text{Initial } N_2 = 1 \quad \& \quad A = 0 \Rightarrow Y = 0)$$

Now

$$Y = 0 \quad \& \quad \text{Clk} = 0 \Rightarrow N_2 = 1$$

Now

$$N_2 = 1 \Rightarrow f'(n+1) = 0$$

$$Y=0 \text{ & (Initial } N_3 = 0) \Rightarrow X=1$$

Now,

$$X=1 \Rightarrow N_1 \geq 0$$


$$N_1 \geq 0 \text{ & } F'(n+1) = 0 \Rightarrow F(n+1) = 1$$

So, by comparing before & after we get

$$F(n) = F(n+1)$$

8) Mod = 13  $\xrightarrow{\text{divide by } 2^3 \text{ to } 2^4}$

No of T flip flop required = 4

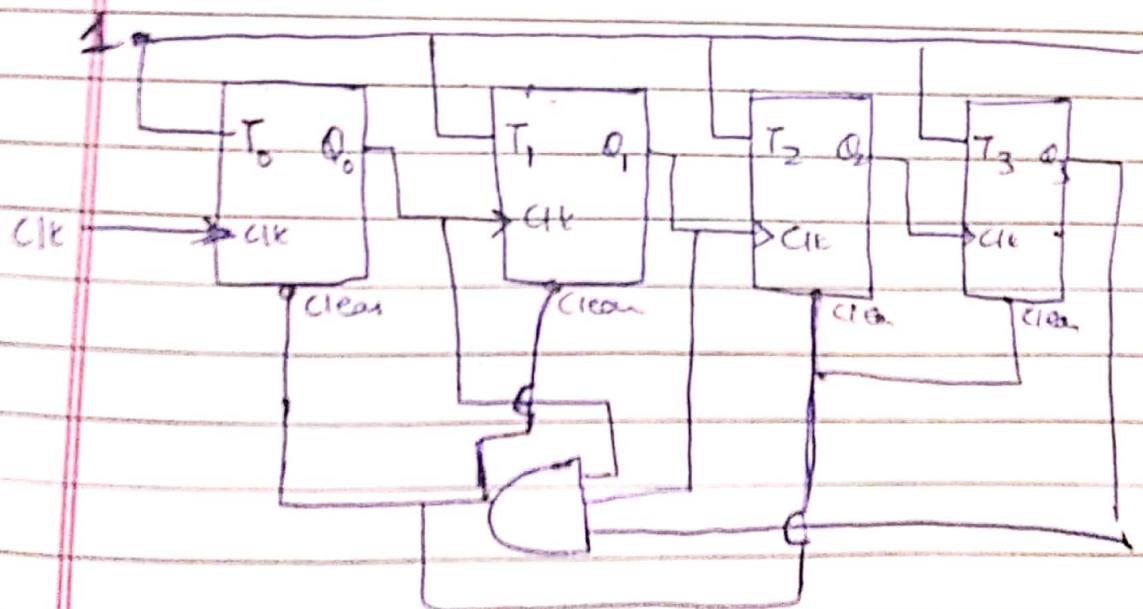

$$13 \Rightarrow 1101$$

Given AND gate to these  
output with value '1'

| Q <sub>4</sub> | Q <sub>3</sub> | Q <sub>2</sub> | Q <sub>1</sub> | Q <sub>0</sub> |
|----------------|----------------|----------------|----------------|----------------|
| 0              | 0              | 0              | 0              | 0              |
| 1              | 0              | 0              | 0              | 1              |
| 2              | 0              | 0              | 0              | 1              |
| 3              | 0              | 0              | 1              | 1              |
| 4              | 0              | 1              | 0              | 0              |
| 5              | 0              | 1              | 0              | 1              |
| 6              | 0              | 1              | 1              | 0              |
| 7              | 0              | 1              | 1              | 1              |
| 8              | 1              | 0              | 0              | 0              |
| 9              | 1              | 0              | 0              | 1              |
| 10             | 1              | 0              | 1              | 0              |
| 11             | 1              | 0              | 1              | 1              |
| 12             | 1              | 1              | 0              | 0              |
| 13             | 1              | 1              | 0              | 1              |
| 14             | 0              | 0              | 0              | 1              |
| 15             | 0              | 0              | 1              | 0              |

At this

Clear will get  
~~use~~ valuemaking ~~Q<sub>4</sub> Q<sub>3</sub> Q<sub>2</sub> Q<sub>1</sub> Q<sub>0</sub>~~


$$\Rightarrow Q_3 Q_2 Q_1 Q_0 = 0000$$

After  
Clear these  
two will start  
from top

9)

$$\text{Mod} \Rightarrow 12 \Rightarrow 2^3 \text{ to } 2^4$$

No of T flip flop required = 4

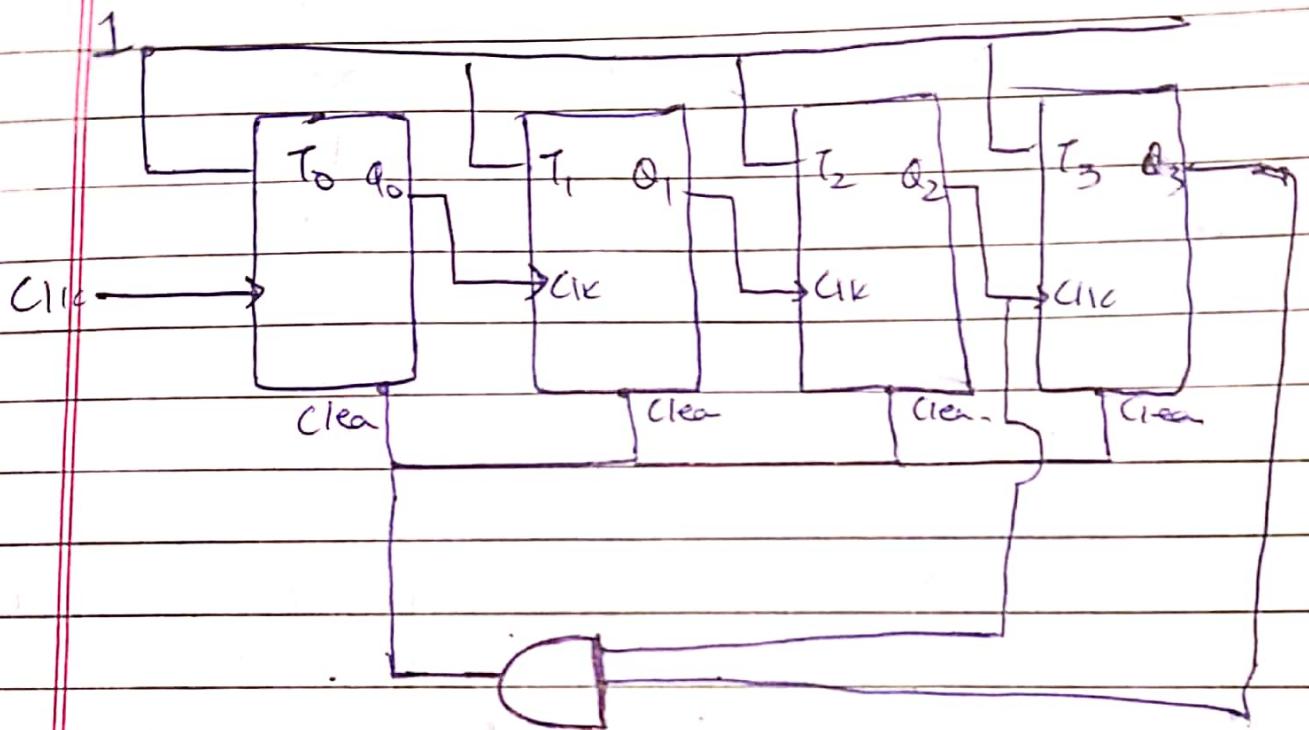

$Q_3 \ Q_2 \ Q_1 \ Q_0$

$12 \Rightarrow 1100$


10) No of JK flip flop required = 3

11) Present state - A

### Excitation Table of JK

| $Q_n$ | $Q_{n+1}$ | J | K |
|-------|-----------|---|---|
| 0     | 0         | 0 | x |
| 0     | 1         | 1 | x |
| 1     | 0         | x | 1 |
| 1     | 1         | x | 0 |

| Present State   | CLK | Next state            | $J_2$ | $K_2$ | $J_1$ , $K_1$ | $J_0$ , $K_0$ |
|-----------------|-----|-----------------------|-------|-------|---------------|---------------|
| $Q_2\ Q_1\ Q_0$ |     | $Q_2^+\ Q_1^+\ Q_0^+$ |       |       |               |               |
| 0 0 0           | 0   | 0 0 1                 | 0     | x     | 0 x           | 1 x           |
| 0 0 0           | 1   | 1 1 1                 | 1     | x     | 1 x           | 1 x           |
| 0 0 1           | 0   | 0 1 0                 | 0     | x     | 1 x           | x y           |
| 0 0 1           | 1   | 0 0 0                 | 0     | x     | 0 x           | x 1           |
| 0 1 0           | 0   | 0 1 1                 | 0     | x     | x 0           | 1 x           |
| 0 1 0           | 1   | 0 0 1                 | 0     | x     | x 1           | 1 x           |
| 0 1 1           | 0   | 1 0 0                 | 1     | x     | x 1           | * 1           |
| 0 1 1           | 1   | 0 1 0                 | 0     | x     | x 0           | x 1           |
| 1 0 0           | 0   | 1 0 1                 | x 0   | 0 x   | 1 x           |               |
| 1 0 0           | 1   | 0 1 1                 | x 1   | 1 x   | 1 x           |               |
| 1 0 1           | 0   | 1 1 0                 | x 0   | 1 x   | x 1           |               |
| 1 0 1           | 1   | 1 0 0                 | x 0   | 0 x   | x 1           |               |
| 1 1 0           | 0   | 1 1 1                 | x 0   | x 0   | 1 x           |               |
| 1 1 0           | 1   | 1 0 1                 | x 0   | x 1   | 1 x           |               |
| 1 1 1           | 0   | 0 0 0                 | x 1   | x 1   | x 1           |               |
| 1 1 1           | 1   | 1 1 0                 | x 0   | x 0   | x 1           |               |

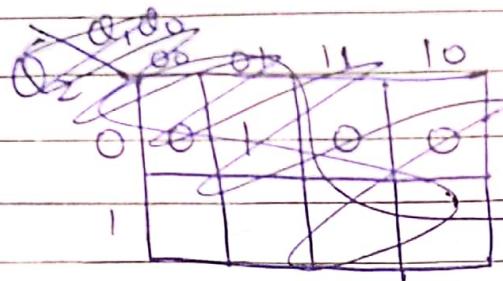K Map for  $J_2$ K Map for  $K_2$ 

|       |       | $Q_2 Q_1$ | $Q_0 \text{ CLK}$ |    |    |   |
|-------|-------|-----------|-------------------|----|----|---|
|       |       | 00        | 01                | 11 | 10 |   |
| $Q_1$ | $Q_2$ | 00        | 0                 | 1  | 0  | 0 |
|       |       | 01        | 0                 | 0  | 0  | 1 |
| 1     | 10    | X         | X                 | X  | X  |   |
| X     | 10    | X         | X                 | X  | X  |   |

|       |       | $Q_2 Q_1$ | $Q_0 \text{ CLK}$ |    |    |   |
|-------|-------|-----------|-------------------|----|----|---|
|       |       | 00        | 01                | 11 | 10 |   |
| $Q_1$ | $Q_2$ | 00        | X                 | X  | X  | X |
|       |       | 01        | 0                 | 0  | 0  | 1 |
| 1     | 10    | 0         | 1                 | 0  | 1  |   |
| X     | 10    | 0         | 1                 | 0  | 1  |   |

$$J_2 = Q_1' Q_0' \text{ CLK} + Q_1 Q_0 C'$$

$$K_2 = Q_1' Q_0' C + Q_1 Q_0 C'$$

|       |       | $Q_2 Q_1$ | $Q_0 \text{ CLK}$ |    |    |   |
|-------|-------|-----------|-------------------|----|----|---|
|       |       | 00        | 01                | 11 | 10 |   |
| $Q_1$ | $Q_2$ | 00        | 0                 | 1  | 0  | 1 |
|       |       | 01        | X                 | X  | X  | X |
| 1     | 11    | X         | X                 | X  | X  |   |
| X     | 10    | 0         | 1                 | 0  | 1  |   |

$$J_1 = Q_0' C + Q_0 C'$$

$$K_1 = Q_0' C + Q_0 C'$$

|       |       | $Q_2 Q_1$ | $Q_0 C$ |    |    |   |
|-------|-------|-----------|---------|----|----|---|
|       |       | 00        | 01      | 11 | 10 |   |
| $Q_1$ | $Q_2$ | 00        | 1       | 1  | X  | X |
|       |       | 01        | 1       | 1  | X  | X |
| 1     | 11    | 1         | 1       | X  | X  |   |
| X     | 10    | 1         | 1       | X  | X  |   |

|       |       | $Q_2 Q_1$ | $Q_0 C$ |    |    |   |
|-------|-------|-----------|---------|----|----|---|
|       |       | 00        | 01      | 11 | 10 |   |
| $Q_1$ | $Q_2$ | 00        | X       | X  | 1  | 1 |
|       |       | 01        | X       | X  | 1  | 1 |
| 1     | 11    | X         | X       | 1  | 1  |   |
| X     | 10    | X         | X       | 1  | 1  |   |

$$J_0 = Q_0'$$

$$K_0 = Q_0$$

11)

Asynchronous BCD using JK

BCD Counter  $\Rightarrow$  0 to 9

11

8v, No of states of 10


$$10 \Rightarrow 2^3 \text{ to } 2^4$$

$$\text{No of JK grp} = 2^3 \times 2^4$$

Truth Table

C<sub>c</sub> D C B A + f(Rest).

|    |   |   |   |   |   |
|----|---|---|---|---|---|
| 0  | 0 | 0 | 0 | 0 | 1 |
| 1  | 0 | 0 | 0 | 1 | X |
| 2  | 0 | 0 | 1 | 0 | X |
| 3  | 0 | 0 | 1 | 1 | 1 |
| 4  | 0 | 1 | 0 | 0 | 1 |
| 5  | 0 | 1 | 0 | 1 | 1 |
| 6  | 0 | 1 | 0 | 1 | 1 |
| 7  | 0 | 1 | 1 | 1 | 1 |
| 8  | 1 | 0 | 0 | 0 | 1 |
| 9  | 1 | 0 | 0 | 1 | 1 |
| 10 | 1 | 0 | 1 | 0 | 0 |
| 11 | 1 | 0 | 1 | 1 | 0 |
| 12 | 1 | 1 | 0 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 | 0 |
| 14 | 1 | 1 | 1 | 0 | 0 |
| 15 | 1 | 1 | 1 | 0 | 0 |

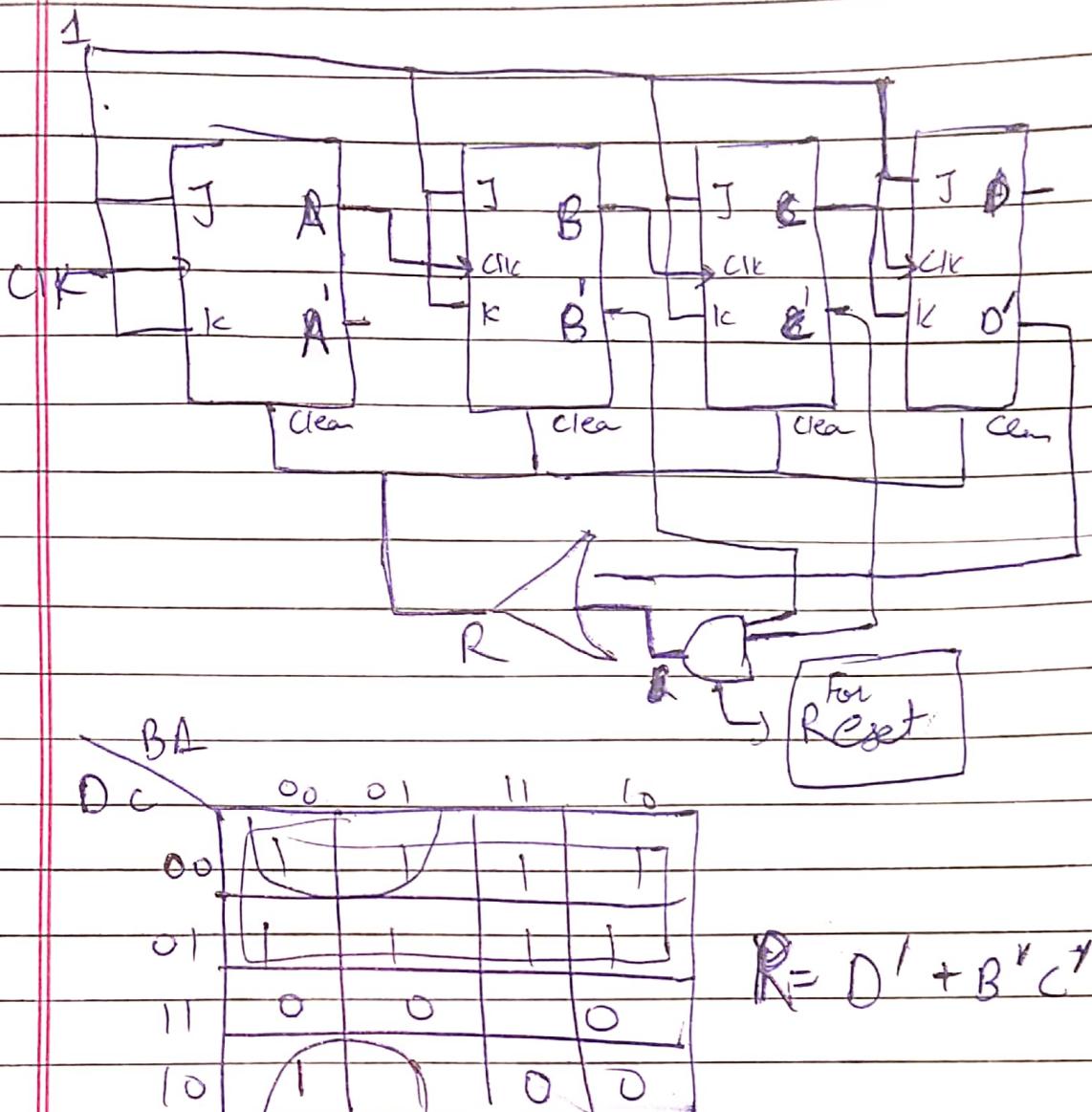

7  
K map to find Reset Gen